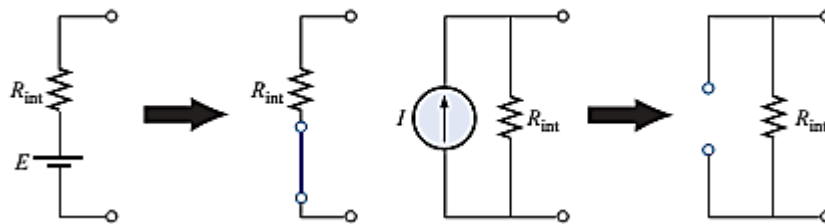



**Superposition theorem:**

The Superposition theorem states that in any network containing more than one source, the **current in**, or the **p.d. across**, any branch can be found by considering each source separately and adding their effects: omitted sources of e.m.f. are replaced by resistances equal to their internal resistances.



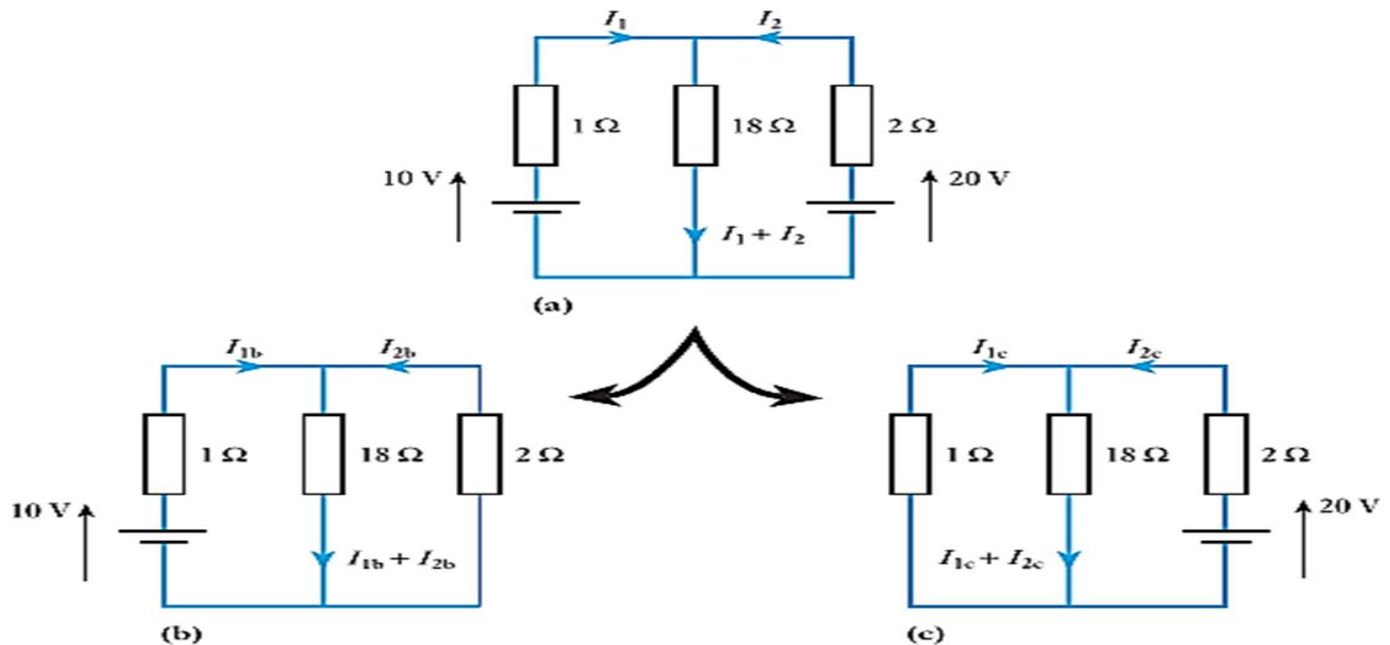**Example1:**

By means of the Superposition theorem, calculate the currents in the network shown in Fig 1



For the (b) arrangement, the total resistance  $R_T$  is

$$1 + \frac{2 \times 18}{2 + 18} = 2.8 \Omega$$

$$\text{thus } I_{1b} = \frac{10}{2.8} = 3.57 \text{ A}$$

$$\text{and } I_{2b} = -\frac{18}{2 + 18} \times 3.57 = -3.21 \text{ A}$$

$$\text{also } I_{1b} + I_{2b} = 3.57 - 3.21 = 0.36 \text{ A}$$

Note: the current  $I_{2b}$  is negative due to the direction in which it has been shown.

$$I_{2b} = \frac{I_T \times R_T}{R_2} = \frac{I_T}{R_2} \times \frac{R_1 \times R_2}{R_1 + R_2} = \frac{I_T \times R_1}{R_1 + R_2}$$

For the (c) arrangement, the total resistance  $R_T$  is

$$2 + \frac{1 \times 18}{1 + 18} = 2.95 \Omega$$

$$\text{thus } I_{2c} = \frac{20}{2.95} = 6.78 \text{ A}$$

$$\text{and } I_{1c} = -\frac{18}{1 + 18} \times 6.78 = -6.42 \text{ A}$$

$$I_{2c} + I_{1c} = 6.78 - 6.42 = 0.36 \text{ A}$$

$$\text{Thus } I_1 = I_{1b} + I_{1c} = 3.57 - 6.42 = -2.85 \text{ A}$$


$$\text{and } I_2 = I_{2b} + I_{2c} = -3.21 + 6.78 = 3.57 \text{ A}$$

$$\text{also } I_1 + I_2 = -2.85 + 3.57 = 0.72 \text{ A}$$

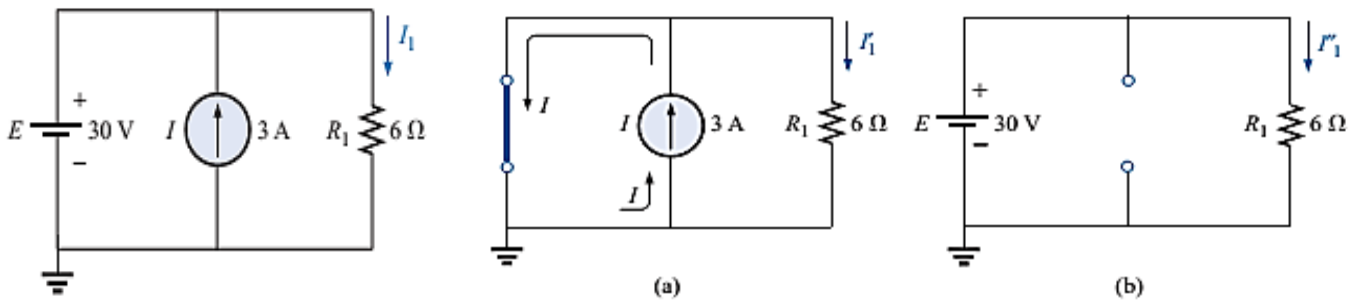**EXAMPLE 2:**

Determine I for the network of Fig2:

Solution: Setting E=0 V for the network of Fig2. Results in the network of Fig. 2(a), where a short-circuit equivalent has replaced the 30-V source.



As shown in Fig2 (a), the source current will choose the short circuit path,  $I_1 = 0A$ . If we applied the current divider rule,

$$I'_1 = \frac{R_{sc} I}{R_{sc} + R_1} = \frac{(0 \Omega) I}{0 \Omega + 6 \Omega} = 0 A$$


Setting I to zero amperes will result in the network of Fig2 (b), with the current source replaced by an open circuit. Applying Ohm's law,

$$I''_1 = \frac{E}{R_1} = \frac{30 V}{6 \Omega} = 5 A$$


$$I_1 = I'_1 + I''_1 = 0 A + 5 A = 5 A$$

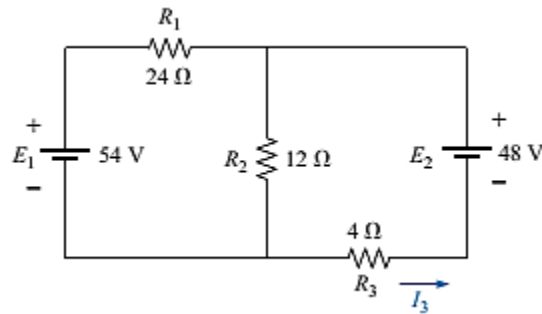**EXAMPLE 3:**

Using superposition, determine the current through the 4Ω resistor of Fig3.



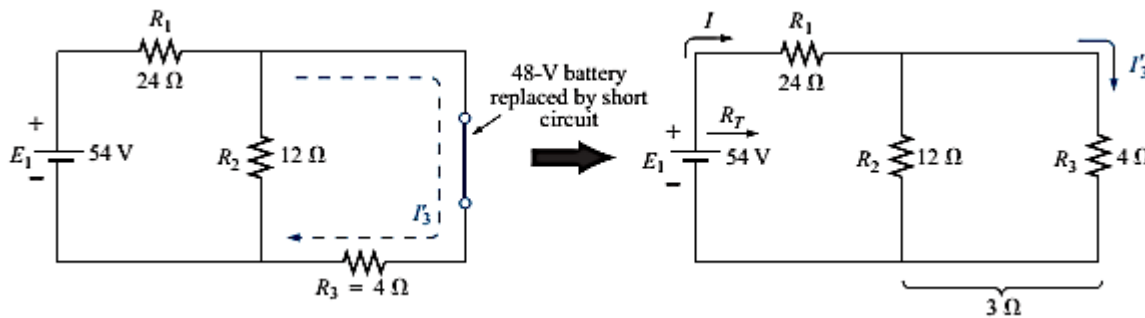Solution: Considering the effects of a 54-V source:




$$R_T = R_1 + R_2 \parallel R_3 = 24 \Omega + 12 \Omega \parallel 4 \Omega = 24 \Omega + 3 \Omega = 27 \Omega$$

$$I = \frac{E_1}{R_T} = \frac{54 \text{ V}}{27 \Omega} = 2 \text{ A}$$

The effect of  $E_1$  on the current  $I_3$  Using the current divider rule

$$I'_3 = \frac{R_2 I}{R_2 + R_3} = \frac{(12 \Omega)(2 \text{ A})}{12 \Omega + 4 \Omega} = \frac{24 \text{ A}}{16} = 1.5 \text{ A}$$

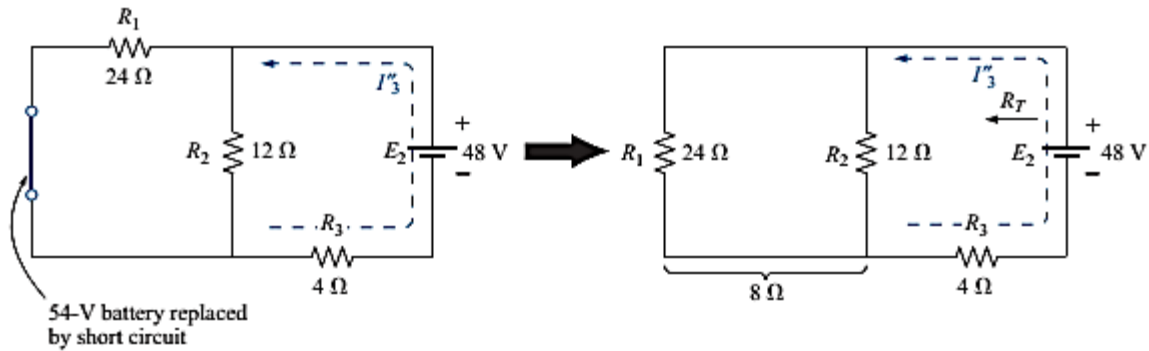Considering the effects of the 48-V source




$$R_T = R_3 + R_1 \parallel R_2 = 4 \Omega + 24 \Omega \parallel 12 \Omega = 4 \Omega + 8 \Omega = 12 \Omega$$

$$I''_3 = \frac{E_2}{R_T} = \frac{48 \text{ V}}{12 \Omega} = 4 \text{ A}$$


The total current through the 4Ω resistor is

$$I_3 = I''_3 - I'_3 = 4 \text{ A} - 1.5 \text{ A} = 2.5 \text{ A} \quad (\text{direction of } I''_3)$$

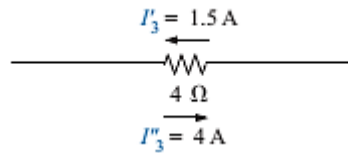

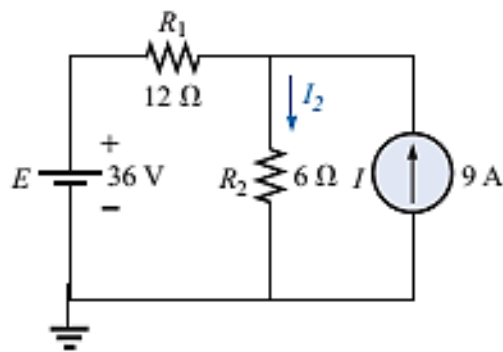
**EXAMPLE 4:**

Using superposition, find the current through the 6Ω resistor of the network of Fig4.




Solutions:

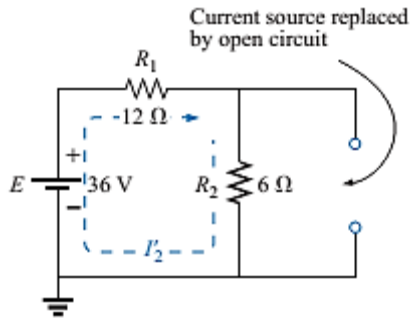Considering the effect of the 36-V source:




$$I'_2 = \frac{E}{R_T} = \frac{E}{R_1 + R_2} = \frac{36 \text{ V}}{12 \Omega + 6 \Omega} = 2 \text{ A}$$

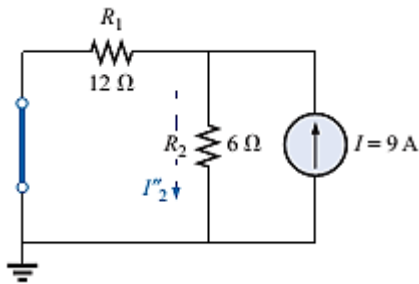Considering the effect of the 9-A source: Applying the current divider rule,



$$I''_2 = \frac{R_1 I}{R_1 + R_2} = \frac{(12 \Omega)(9 \text{ A})}{12 \Omega + 6 \Omega} = \frac{108 \text{ A}}{18} = 6 \text{ A}$$

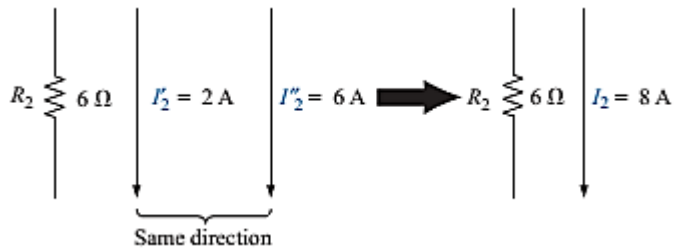
The total current through the 6Ω resistor is




$$I_2 = I'_2 + I''_2 = 2 \text{ A} + 6 \text{ A} = 8 \text{ A}$$

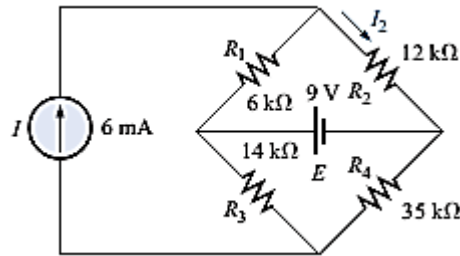**EXAMPLE 5:**

Using the principle of superposition, find the current  $I_2$  through the 12-k $\Omega$  resistor of Fig5



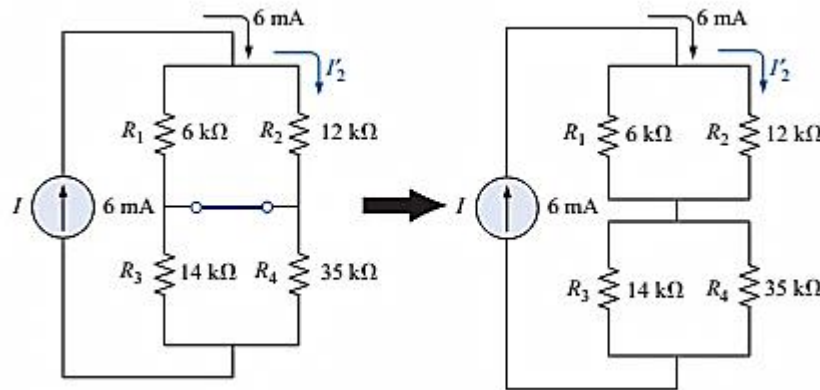
Solution: Considering the effect of the 6-mA current source:



Current divider rule:

$$I'_2 = \frac{R_1 I}{R_1 + R_2} = \frac{(6 \text{ k}\Omega)(6 \text{ mA})}{6 \text{ k}\Omega + 12 \text{ k}\Omega} = 2 \text{ mA}$$

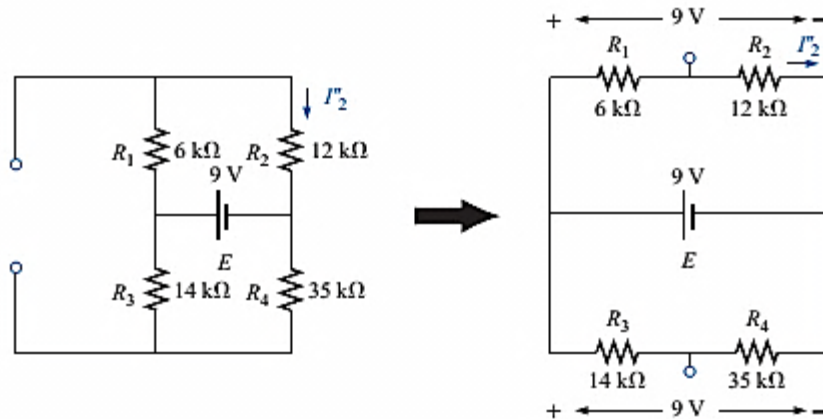Considering the effect of the 9-V voltage source:




$$I''_2 = \frac{E}{R_1 + R_2} = \frac{9 \text{ V}}{6 \text{ k}\Omega + 12 \text{ k}\Omega} = 0.5 \text{ mA}$$

Since the two have the same direction through R2, the desired current is the sum of the two:


$$\begin{aligned} I_2 &= I'_2 + I''_2 \\ &= 2 \text{ mA} + 0.5 \text{ mA} \\ &= 2.5 \text{ mA} \end{aligned}$$

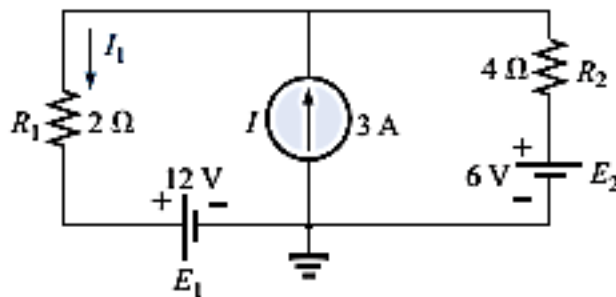**EXAMPLE 6:**


Find the current through the 2Ω resistor of the network of Fig6. The presence of three sources will result in three different networks to be analyzed.






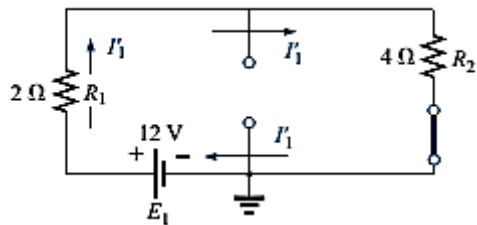
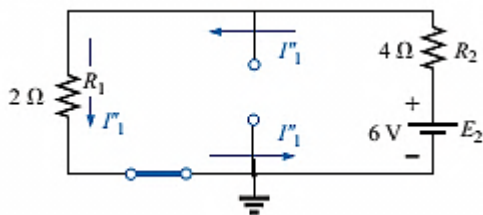
$$I'_1 = \frac{E_1}{R_1 + R_2} = \frac{12\text{ V}}{2\ \Omega + 4\ \Omega} = \frac{12\text{ V}}{6\ \Omega} = 2\text{ A}$$



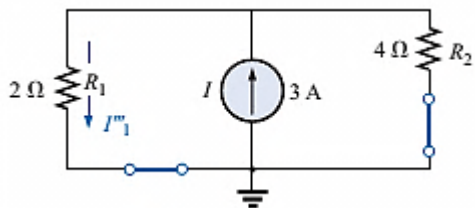
$$I''_1 = \frac{E_2}{R_1 + R_2} = \frac{6\text{ V}}{2\ \Omega + 4\ \Omega} = \frac{6\text{ V}}{6\ \Omega} = 1\text{ A}$$




$$I'''_1 = \frac{R_2 I}{R_1 + R_2} = \frac{(4\ \Omega)(3\text{ A})}{2\ \Omega + 4\ \Omega} = \frac{12\text{ A}}{6} = 2\text{ A}$$

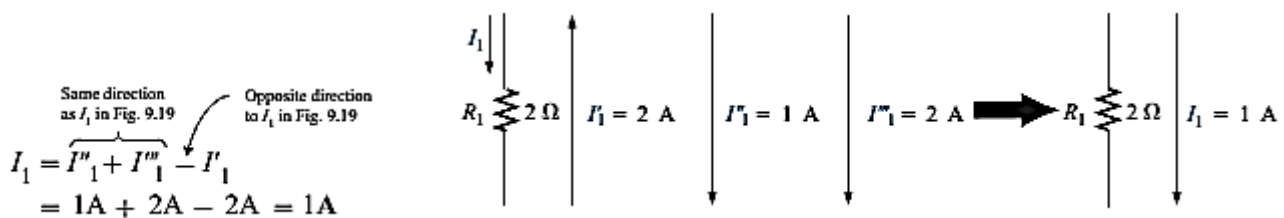The total current through the 2Ω resistor appears



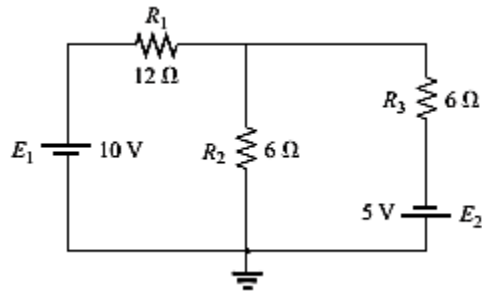
### PROBLEMS


- Using superposition, find the current through each resistor of the network of Fig. 1



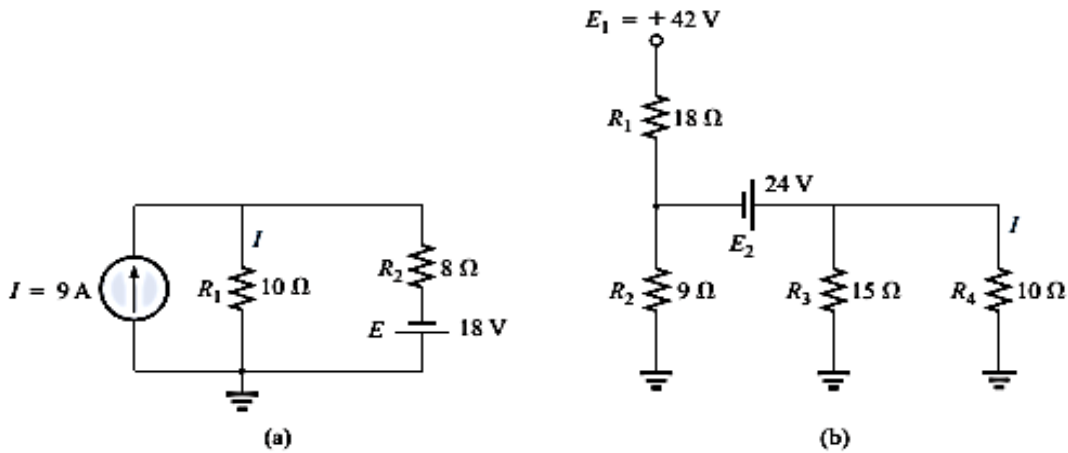2. Using superposition, find the current  $I$



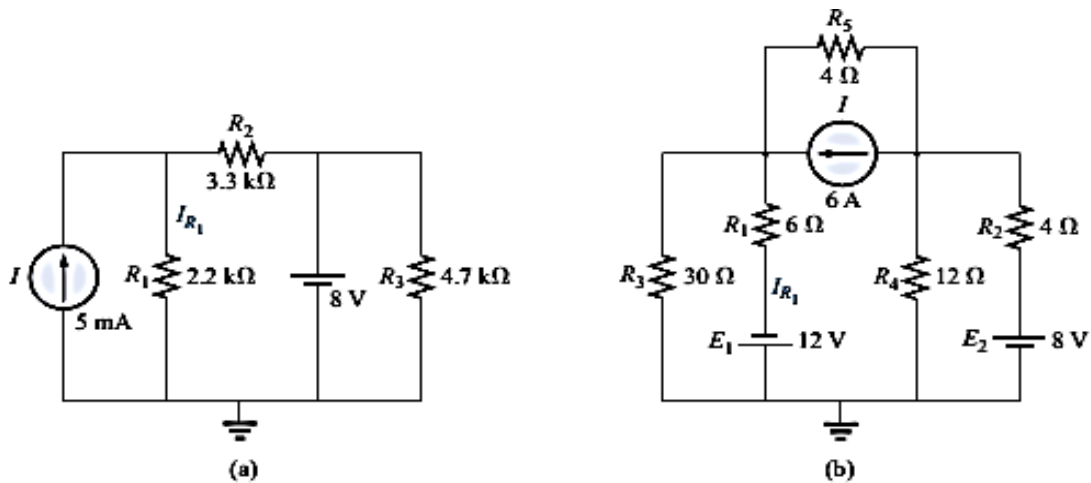3. Using superposition, find the current through  $R_1$  for each network of Fig3.



4. Using superposition, find the voltage  $V_2$  for the network of Fig4.

