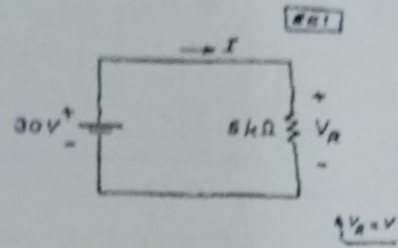


اسس كهرباء  
قسم هندسة تقنيات التبريد والتكييف  
المرحلة الاولى  
المحاضرة الثانية  
م.م. سارة جعفر شاوي

Example  
In the circuit shown, calculate the current  $I$ , the conductance  $G$ , and the power  $P$



Solution

- The current  $I = \frac{V_R}{R} = \frac{30}{5 \times 10^3} = 6 \times 10^{-3} = 6 \text{ mA}$

- The conductance  $G = \frac{1}{R} = \frac{1}{5 \times 10^3} = 0.2 \times 10^{-3} = 0.2 \text{ mS}$

- The power  $P = V_R I = 30 (6 \times 10^{-3}) = 180 \text{ mW}$

or  
 $P = I^2 R = (6 \times 10^{-3})^2 (5 \times 10^3) = 180 \text{ mW}$

or  
 $P = V_R^2 G = (30)^2 (0.2 \times 10^{-3}) = 180 \text{ mW}$


### 1.2.2 Nodes, branches and loops

\* A branch represents a single element in the electric circuit, such as a voltage source or a resistor etc...

\* A node represents the point of connection between two or more branches.

\* A loop is any closed path in a circuit.

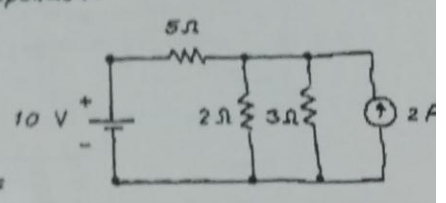Example  
For the circuit shown, determine the number of branches, nodes and the independent loops.



Solution Since there are 5 elements

$\Rightarrow$  Number of branches = 5      10V, 5Ω, 2Ω, 3Ω, and 2A

Number of nodes = 3 (as shown in the figure).  
3 nodes

نقطة على التوالي



→ There are 3 nodes: a, b and c

\* The number of the independent loops = 3

→ loop 1 or loop abc: contains (10V, 5Ω, 2Ω)

→ loop 2 or loop bc b: contains (2Ω, 3Ω)

→ loop 3 or loop bc b: contains (3Ω, 2A)

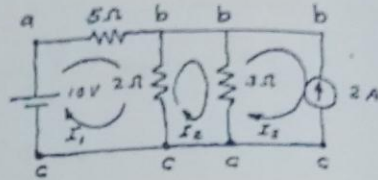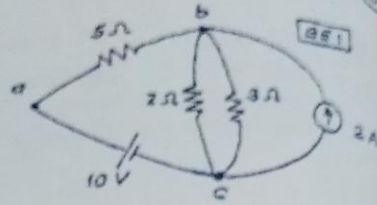

Notes

—: There are more than 3 (dependent) loops in this example, we had only calculated the INDEPENDENT loops which are only 3.

IN GENERAL; Any circuit with b branches, n nodes and l independent loops, the following fundamental theorem of network topology

$$b = l + n - 1$$

\* Two or more elements are in SERIES if they are cascaded sequentially and consequently carry the SAME current.

\* Two or more elements are in PARALLEL if they are connected to the same two nodes and have consequently the same VOLTAGE across them.

### 1.2.3 Kirchoff's Laws (1847)

قانون كيرشوف للتيار \* Kirchoff's current law (KCL); states that the algebraic sum of all current entering a node is zero or: The sum of currents entering a node is equal to the sum of currents leaving that node.


$$\sum_{n=1}^N I_n = 0$$

or

$$\sum_{m=1}^M I_m = \sum_{n=1}^N I_n$$

where  $I_m$  are the currents entering the node and  $I_n$  are the currents leaving the node.

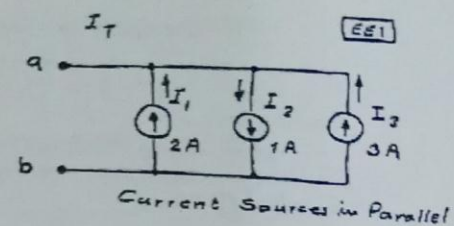Example  
 For the network shown, calculate the total current  $I_T$




Solution

According to KCL;

$$I_T = I_1 - I_2 + I_3$$

$$= 2 - 1 + 3 = \underline{\underline{5A}}$$

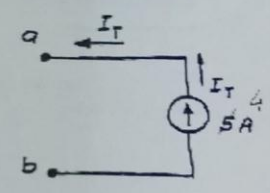∴ The equivalent circuit for the network can be as shown ⇒



\* Kirchoff's Voltage Law (KVL); states that the algebraic sum of all voltages around a closed path (or loop) is zero.  
 قانون Kirchhoff للتيار


∴ Mathematically KVL states that:

$$\sum_{m=1}^M V_m = 0$$

where  $M$  is the number of voltages in the loop (or the number of branches in the loop), and  $V_m$  is the  $m$ th voltage.

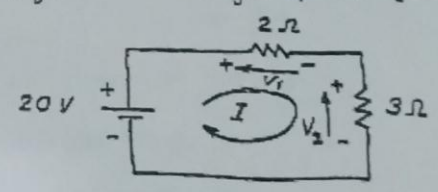Example

For the circuit shown, find the voltages  $V_1$  and  $V_2$



Solution

$$V_1 = 2I$$

$$V_2 = 3I$$

From KVL:

$$\sum V = 0 \Rightarrow 20 - V_1 - V_2 = 0 \Rightarrow 20 = 3I + 2I$$


$$\Rightarrow 5I = 20 \Rightarrow I = 4A$$

$$\therefore V_1 = 2I = \underline{\underline{8V}} \quad \text{and} \quad V_2 = 3I = \underline{\underline{12V}}$$

Tutorial Sheet No 1  
Basic Concepts & Basic Laws

T31

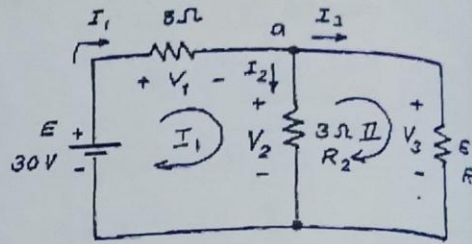Example Using Kirchoff's laws.  
find the currents and voltages in  
the circuit shown.



Solution:

ملاحظة: المطلوب في المسألة إيجاد كل من  
 $I_1, I_2, I_3, V_1, V_2, V_3$   
باستخدام قانون كيرشوف

\* Using Ohm's law:

$$\begin{aligned} V_1 &= I_1 R_1 = 8 I_1 \\ V_2 &= I_2 R_2 = 3 I_2 \\ V_3 &= I_3 R_3 = 6 I_3 \end{aligned}$$

\* Applying KCL at node a:

$$I_1 = I_2 + I_3 \Rightarrow I_1 - I_2 - I_3 = 0 \quad \text{Eq(1)}$$

\* Applying KVL to loop 1;

$$\begin{aligned} E - V_1 - V_2 &= 0 \Rightarrow 30 - V_1 - V_2 = 0 \\ \Rightarrow 30 - 8 I_1 - 3 I_2 &= 0 \\ \therefore I_1 &= \frac{30 - 3 I_2}{8} \quad \text{Eq(2)} \end{aligned}$$

\* Applying KVL to loop 2;

$$\begin{aligned} V_2 - V_3 &= 0 \Rightarrow V_2 = V_3 \\ \therefore 6 I_3 &= 3 I_2 \\ \therefore I_3 &= \frac{I_2}{2} \quad \text{Eq(3)} \end{aligned}$$

$\Rightarrow$  From Eq(1), Eq(2) & Eq(3)

$$\frac{30 - 3 I_2}{8} - I_2 - \frac{I_2}{2} = 0 \Rightarrow I_2 = \underline{\underline{2 A}}$$

$$\text{and } I_1 = \frac{30 - 3 I_2}{8} = \frac{30 - 3(2)}{8} = \underline{\underline{3 A}}$$

$$I_3 = \frac{I_2}{2} = \frac{2}{2} = 1 A$$

$\Rightarrow \therefore V_1 = 8I_1 \Rightarrow \therefore V_1 = 8(3) = 24V$  T.S.1

Similarly  $V_2 = 3I_2 = 3(2) = 6V$

and  $V_3 = 6I_3 = 6(1) = 6V$

للتأكد من صحة الحل :

$I_1 = I_2 + I_3$   
 $3 = 2 + 1 \Rightarrow 3 = 3$

كذلك فان تطبيق قانون كيرشوف للعولمة على المسار المقطوع رسمه  $\Rightarrow$  يتبين ما يلي :


$E = V_1 + V_2$   
 $\therefore 30 = 24 + 6$

$\therefore 30 = 30$

$\therefore$  الحل صحيح

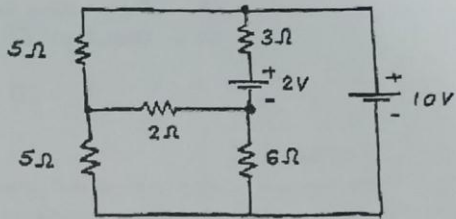Example

Determine the number of branches, nodes and independent loops in the circuit shown.



Solution


\* There are 7 element  $\Rightarrow$  no. of branches = 7  
 $\Rightarrow b = 7$

\* There are 5 nodes as shown in the figure :  
 $\Rightarrow n = 5$

\* There are 3 independent loops :  
 $\Rightarrow l = 3$

$\therefore b = l + n - 1$  is satisfied

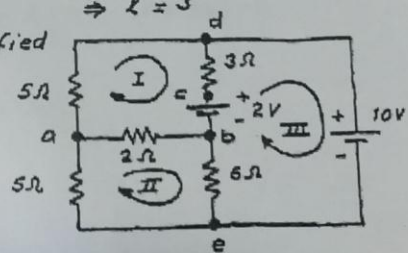
Since  $7 = 3 + 5 - 1$   
 $\Rightarrow 7 = 7$



**Practice Problem**

Identify all nodes, branches and independent loops in the circuit shown in the figure.

751

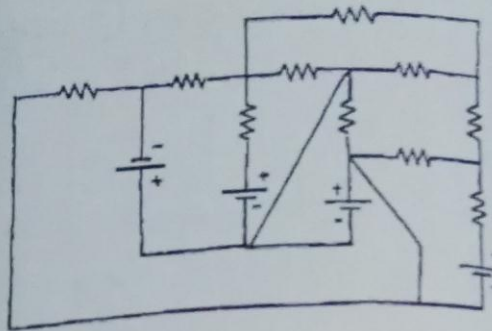

**Answer:**

no. of nodes = 8       $n = 8$   
 no. of branches = 14       $b = 14$   
 no. of independent loops = 7       $l = 7$


Check. Does this satisfy the fundamental theorem of network topology?

$$b = l + n - 1 = 7 + 8 - 1 = 14 \quad \text{YES}$$

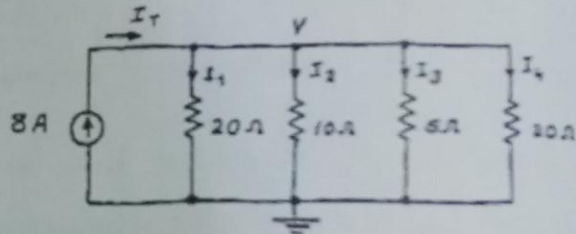**Example**

Determine all currents and voltages in the circuit of the figure shown.

$l = 4$   
 $b = 5$   
 $b = l + n - 1$   
 $5 = 4 + n - 1$   
 $5 = 3 + n \Rightarrow n = 5 - 3 = 2$



**Solution**

KCL  $\Rightarrow$

$$I_T = I_1 + I_2 + I_3 + I_4 \Rightarrow 3 = I_1 + I_2 + I_3 + I_4$$

Ohm's law

$$\begin{aligned}
 V &= 20 I_1 & \Rightarrow I_1 &= V/20 \\
 &= 10 I_2 & I_2 &= V/10 \\
 &= 5 I_3 & I_3 &= V/5 \\
 &= 20 I_4 & I_4 &= V/20
 \end{aligned}$$

Substituting in the current equation:

T41

$$\Rightarrow 8 = \frac{V}{20} + \frac{V}{10} + \frac{V}{5} + \frac{V}{20}$$

$$\therefore 160 = V + 2V + 4V + V$$

$$160 = 8V$$

$$\therefore \underline{V = 20 \text{ Volts}}$$

$$\therefore I_1 = \frac{V}{20} = \frac{20}{20} = 1 \text{ A}$$

$$I_2 = \frac{V}{10} = \frac{20}{10} = 2 \text{ A}$$

$$I_3 = \frac{V}{5} = \frac{20}{5} = 4 \text{ A}$$

$$I_4 = \frac{V}{20} = \frac{20}{20} = 1 \text{ A}$$

Check

$$I_T = I_1 + I_2 + I_3 + I_4$$

$$8 = 1 + 2 + 4 + 1$$

$$8 = 8 \quad \checkmark$$